

• Candidates should be able to :

- State Kirchhoff's second law and appreciate that it is a consequence of conservation of energy.
- Apply Kirchhoff's first and second laws to circuits.
- Select and use the equation for the total resistance of two or more resistors in series.
- Recall and use the equation for the total resistance of two or more resistors in parallel.
- Solve circuit problems involving **series** and **parallel** circuits with one or more sources of e.m.f.
- Explain that all sources of e.m.f have an **internal resistance**.
- Explain the meaning of the term **terminal pd**.
- Select and use the equations :

$$E = I(R + r)$$

And  $E = V + Ir$

**LAW 1 (K1)**

The sum of the currents flowing into any point in a Circuit is equal to the sum of the currents flowing Out of the point.


i.e.  $\sum I_{in} = \sum I_{out}$

Greek letter 'sigma', which means 'the sum of all'.

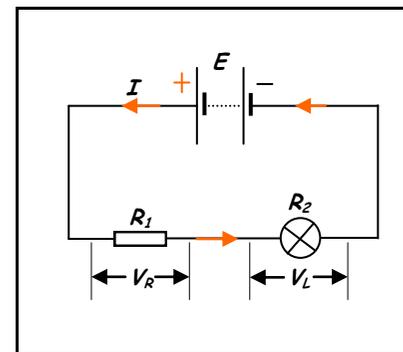**LAW 2 (K2)**

Consider the circuit shown opposite.

As charge flows through the battery (of e.m.f.  $E$ ), electrical energy is supplied to each coulomb. The charge then flows through the resistor of resistance ( $R_1$ ) and through the filament lamp of resistance ( $R_2$ ). In each of these components the electrical energy is converted to heat and heat and light energy respectively.



Energy supplied per coulomb by The battery (i.e. the e.m.f.) = The sum of the energies converted per coulomb in each component (i.e. the sum of the pd's)

$$E = V_R + V_L$$

And since the current ( $I$ ) is the same at each point in a **SERIES** circuit :

$$E = IR_1 + IR_2$$

This equation expresses **KIRCHHOFF'S SECOND LAW (K2)** which states that :

In any closed loop in a circuit, the sum of the emf's is equal to the sum of the pd's around the loop.

- As we have seen from our energy analysis of a simple circuit, If a unit charge follows a closed path in a circuit :

Total energy supplied = Total energy dissipated  
to the charge. by the charge.


i.e. **KIRCHHOFF'S SECOND LAW** is a consequence  
Of the **PRINCIPLE OF CONSERVATION OF ENERGY.**

**EXAMPLES OF THE USE OF KIRCHHOFF'S LAWS  
IN THE SOLUTION OF CIRCUIT PROBLEMS**

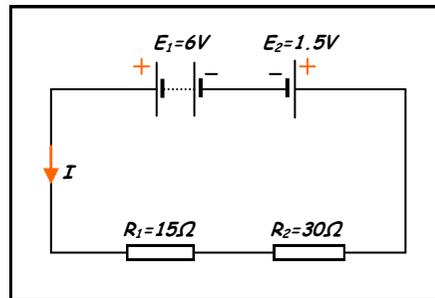- (1) Use Kirchhoff's Law 2 to determine the current (I) in the circuit shown opposite.

Net emf = sum of the pd's  
 $E_1 - E_2 = IR_1 + IR_2$   
 $6 - 1.5 = (I \times 15) + (I \times 30)$   
 $4.5 = 45I$

$I = \frac{4.5}{45} = \boxed{0.1 \text{ A}}$



- (2) Use Kirchhoff's Laws to calculate the currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown opposite.

- Mark in the currents and label the closed loops **ABCDEF** as shown.

- Applying Kirchhoff 1 to point **F**

$I_3 = I_1 + I_2 \dots\dots\dots (1)$

- Applying Kirchhoff 2 to loop **FCDEF**

$4 = 20 I_3 \quad \text{So } I_3 = 4/20 = \boxed{0.2 \text{ A}}$

- Applying Kirchhoff 2 to loop **ABCFA**


$12 = 20 I_3 + 5 I_1 = (20 \times 0.2) + 5 I_1 = 4 + 5 I_1$

$I_1 = 8/5 = \boxed{1.6 \text{ A}}$

- Substituting for  $I_1$  &  $I_2$  in equation (1)

$0.2 = 1.6 + I_2 \quad \text{So } I_2 = 0.2 - 1.6 = \boxed{-1.4 \text{ A}}$

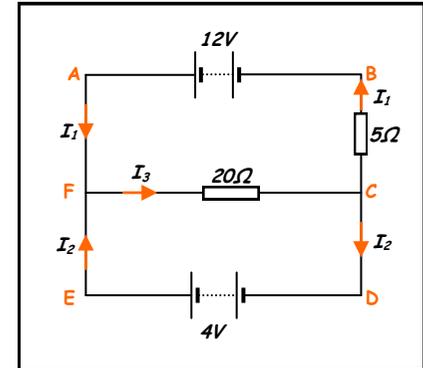The negative sign tells us that  $I_2$  flows in a direction opposite to that chosen.




- (3) The circuit diagram opposite shows a battery charger of emf 5.5 V and internal resistance 1.0 Ω being used to recharge a cell of emf 1.2 V and internal resistance 0.20 Ω.

Use Kirchhoff's Law 2 to determine the charging current I.

- Applying Kirchhoff 2 to the loop

$5.5 - 1.2 = (I \times 1.0) + (I \times 0.20)$   
 $4.3 = 1.2 I$


$I = 4.3/1.2 = \boxed{3.58 \text{ A}}$

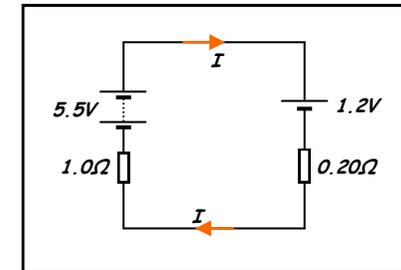

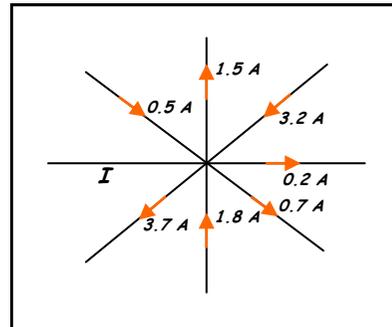**PRACTICE QUESTIONS (1)**

1 The diagram opposite shows a junction in a circuit.


Use Kirhhoff's First Law ( $\Sigma I_{in} = \Sigma I_{out}$ ) to determine the size and direction of the current I.




2 Use Kirhhoff's Second Law to Calculate :

(a) The pd across resistor R.


(b) The value of R.

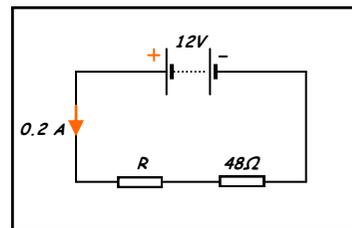

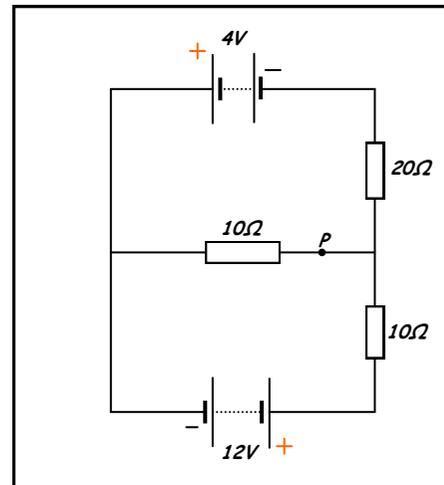3 Use Kirhhoff's laws to determine the size and direction of the **current at point P** in the circuit shown opposite.



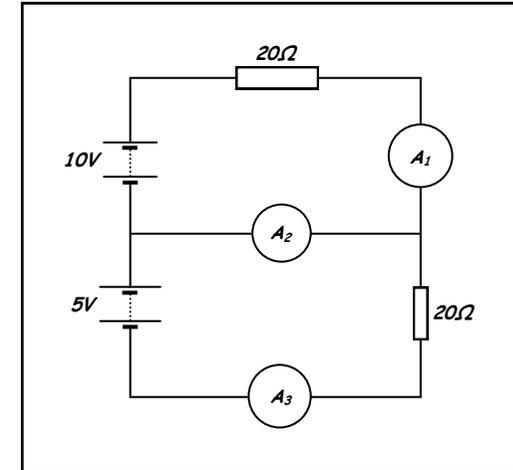
4 Use Kirhhoff's laws to determine the **current readings** shown on the ammeters ( $A_1$ ,  $A_2$  &  $A_3$ ) in the circuit shown opposite.



**COMBINATION OF RESISTORS**

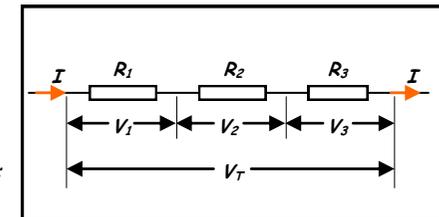**RESISTORS IN SERIES**

Consider three resistors of resistance  $R_1$ ,  $R_2$  and  $R_3$  connected **IN SERIES** as shown opposite.



• According to Kirhhoff's Law 1 :  
The current ( $I$ ) is the same in each resistor.

• Since energy is conserved :  
Total pd across the combination = The sum of the pds across each resistor

(And since  $V = IR$ )  
From which :

$$V_T = V_1 + V_2 + V_3$$

$$IR_T = IR_1 + IR_2 + IR_3$$


$$R_T = R_1 + R_2 + R_3$$

For any number of resistors connected **IN SERIES**, the **TOTAL RESISTANCE ( $R_T$ )** is given by :

$$R_T = R_1 + R_2 + R_3$$

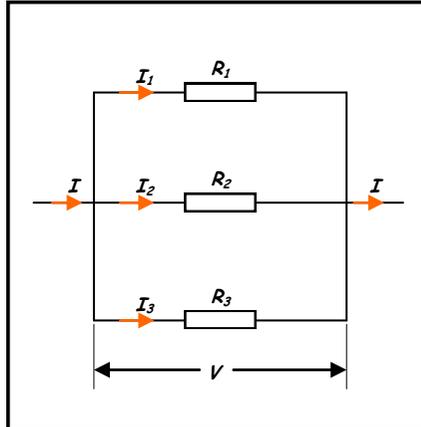**RESISTORS IN PARALLEL**

Consider three resistors of resistance  $R_1$ ,  $R_2$  and  $R_3$  connected **IN PARALLEL** as shown opposite.



- According to Kirchoff's Law 1

$$I = I_1 + I_2 + I_3 \dots \dots \dots (1)$$

- The pd across each resistor =  $V$

- From the definition of resistance :

$$I = V/R$$

And applying this to equation (1) :

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

From which :  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

For any number of resistors connected **IN PARALLEL**, the **TOTAL RESISTANCE ( $R_T$ )** of the combination is given by :

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

- For resistors connected **IN PARALLEL** :
  - The **LOWEST** value resistors carry the **GREATEST** proportion of the current.
  - The **TOTAL RESISTANCE** of the combination is **LESS** than the **SMALLEST** resistance in the combination.


- **SPECIAL CASE FOR RESISTORS IN PARALLEL**

If ( $N$ ) resistors having the same resistance ( $R$ ) are connected **IN PARALLEL**, the **TOTAL RESISTANCE ( $R_T$ )** is given by :

$$R_T = \frac{R}{N}$$

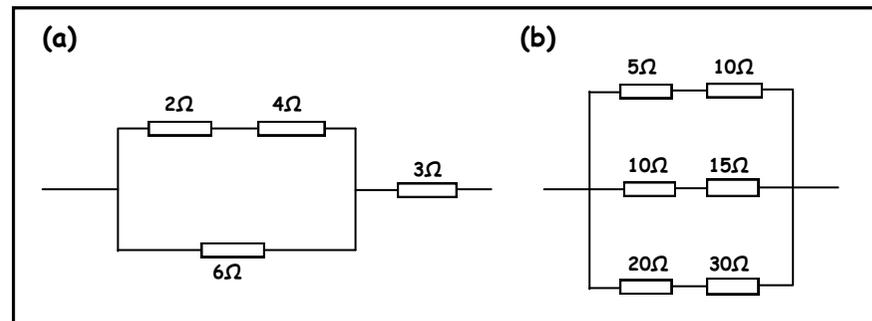**PRACTICE QUESTIONS (2)**

- 1 Calculate the **total resistance** of the resistor combinations shown below :




- 2 (a) What resistor value needs to be connected **in parallel** with a **20 Ω** resistor to give a combined **total resistance** of **10 Ω** ?  
 (b) You are provided with several **100 Ω** resistors. How could you combine the **minimum number** of these resistors to give a **total resistance** of **250 Ω** ?

- 3 You are provided with a **400 Ω** resistor and **two 200 Ω** resistors. Calculate the **total resistances** which may be obtained by connecting **some** or **all** of these resistors in various combinations.


4 For the resistor network shown calculate :

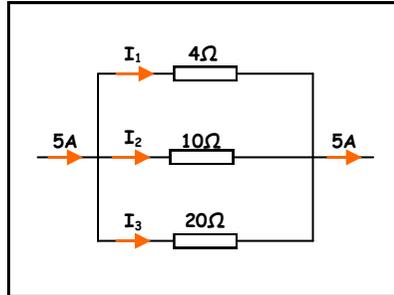- (a) The **total resistance** of the combination.
- (b) The **pd ( $V$ )** across each resistor.
- (c) The value of the **currents ( $I_1$ ,  $I_2$  &  $I_3$ )** through each of the resistors.




5 For the circuit shown opposite, calculate :

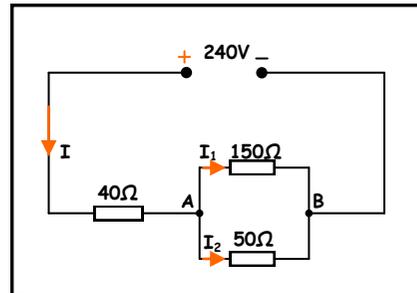- (a) The **resistance ( $R_{AB}$ )** of the parallel combination.
- (b) The **total resistance ( $R_T$ )** of the circuit.
- (c) The currents  **$I$ ,  $I_1$  and  $I_2$** .
- (d) The pd across the  **$40\ \Omega$**  resistor.




6 In the circuit shown opposite the voltmeter gives a reading of **8 V**. Calculate :

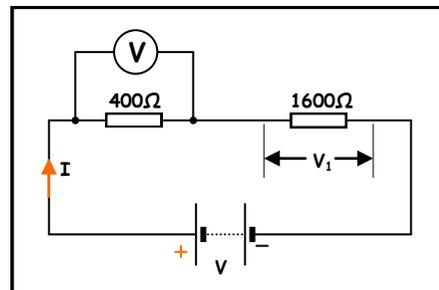- (a) The **pd's  $V$  and  $V_1$** .
- (b) The **pd across the  $1600\ \Omega$**  resistor when the voltmeter is disconnected.



- All sources of emf have some **INTERNAL RESISTANCE ( $r$ )**, since they are made from materials (e.g. metal wires, electrodes, chemical electrolytes) which have some electrical resistance.

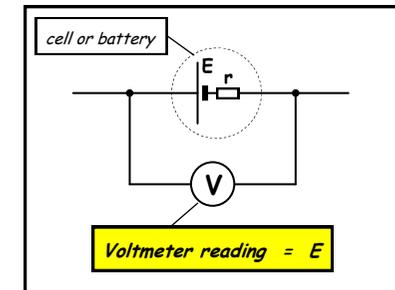- If a voltmeter is connected across the terminals of an electrical supply (e.g. a cell or battery), it indicates what is called the **TERMINAL PD ( $V$ )** of the cell or battery.




If the cell or battery is not part of an external circuit and the voltmeter is 'ideal' (i.e. it has infinite resistance), then **zero current** is drawn and :

**voltmeter reading = cell emf ( $E$ )**

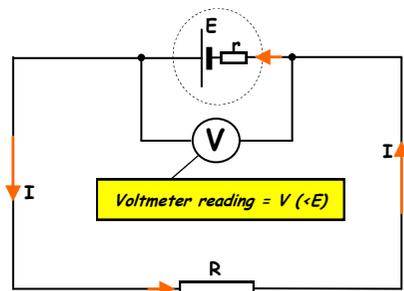**The emf ( $E$ ) of a cell or battery can be defined as its TERMINAL PD when it is NOT supplying a current.**

If an external circuit is connected to the cell or battery (or the voltmeter is not perfect and draws some current), the reading on the voltmeter drops to a value less than E.



This is because when there is a current through the cell, some of its energy is converted into heat by the cell's internal resistance.

The decrease in voltage is called the '**LOST VOLTS**' of the cell and it is proportional to the current.

The reading (V) which is < E indicated by the voltmeter is the **TERMINAL PD** of the cell and also the **pd across the resistor R**.

Applying Kirchhoff's Law 2 to the circuit :

Emf of the cell = terminal pd + pd across the internal resistance  
(= pd across R)

$$E = V + Ir$$

$$E = IR + Ir = I(R + r)$$


$$I = \frac{E}{(R + r)}$$

- A good estimate of the emf (E) of a cell, battery or power supply may be obtained by simply measuring the terminal pd with a **DIGITAL VOLTMETER** (These have a high resistance and will therefore only draw a very small current).

Value of E given by the digital voltmeter =  V

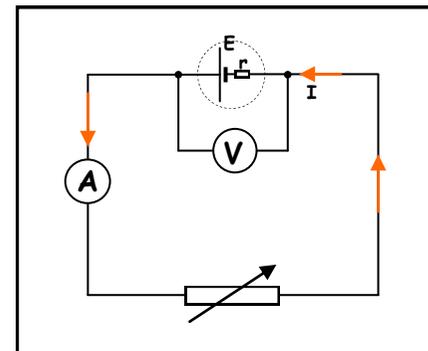**PROCEDURE**

- The circuit shown opposite is used to obtain a more accurate determination of the **emf (E)** of a cell as well as its **internal resistance (r)**.



Corresponding values of the **current (I)** in the cell and **pd (V)** across the cell are obtained by adjusting the variable resistor. The results are recorded in the table shown below.


**RESULTS**

PD (V)/V									
Current (I)/A									

**GRAPH**

- When a graph of pd (V) is plotted, a best fit straight line should be obtained as shown opposite.

**NOTE** : In practice the graph is curved because ( $r$ ) changes as the current ( $I$ ) increases.

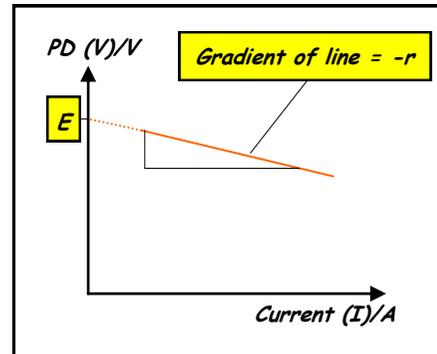**ANALYSIS OF GRAPH**

- The equation which links **EMF (E)**, **TERMINAL PD (V)**, **CURRENT(I)** and **INTERNAL RESISTANCE (r)** is :

$$E = V + Ir$$

Rearranging :

$$V = -Ir + E$$

Comparing with the equation

For a straight line :

$$y = mx + c$$

It can be seen that :

- Intercept on the y-axis =  $E =$   V
- Gradient of the V/I graph =  $r =$    $\Omega$

**SOME EFFECTS OF INTERNAL RESISTANCE**

- Low voltage sources** from which **large currents** are drawn (e.g. car batteries) should have **LOW internal resistance**, otherwise their terminal PD ( $V = E - Ir$ ) would be **very low**.
- High voltage sources** (e.g. 5 kV supplies which are sometimes used in schools) have a **HIGH internal resistance** so as to **limit the current supplied** should they be short-circuited accidentally.
- The headlamps on a car will dim if the vehicle is started while they are switched on. This is because the starter motor draws a **large current** and this causes the **battery terminal PD** ( $V = E - Ir$ ) to drop sharply.
- In order to get an **efficient transfer of energy** from a source of emf to an external component of resistance ( $R$ ), the internal resistance ( $r$ ) of the source  $\ll R$ .

**PRACTICE QUESTIONS (3)**

- A battery of emf **4.5 V** and internal resistance **1.5  $\Omega$**  is connected to a **10  $\Omega$**  fixed resistor. Draw a circuit diagram of the arrangement and calculate the **current** in the circuit.
- A battery of emf **15 V** and internal resistance **1.2  $\Omega$**  is connected to an **8  $\Omega$**  resistor. Calculate :
  - The **total resistance** of the circuit.
  - The **current** through the battery.
  - The "lost volts"
  - The battery's **terminal pd**.

3 A battery of emf ( $E$ ) and internal resistance ( $r$ ) was connected in series with a variable resistor of resistance ( $R$ ) and an ammeter. If the ammeter reading was  $2.0\text{ A}$  when  $R$  was set to  $4.0\ \Omega$  and it dropped to  $1.5\text{ A}$  when  $R$  was set to  $6.0\ \Omega$ , calculate the values of  $E$  and  $r$ .

4 The pd across the terminals of a battery is found to be  $3.0\text{ V}$  when it is measured using a **very high resistance** voltmeter. The battery is then connected to a  $10\ \Omega$  resistor and its terminal pd drops to  $2.8\text{ V}$ . Calculate the **internal resistance** of the battery.

5 A **high resistance** voltmeter gives a reading of  $1.5\text{ V}$  when connected to a dry cell on "**open circuit**". When the cell is connected to a lamp of resistance  $R$ , there is a current of  $0.30\text{ A}$  and the voltmeter reading drops to  $1.2\text{ V}$ . Calculate :

(a) The **emf** of the cell.

(b) The **internal resistance** of the cell.

(c) The value of the **resistance R**.

6 A car battery has an emf of  $12\text{ V}$  and an internal resistance of  $0.05\ \Omega$ . The current drawn by the starter motor is  $96\text{ A}$ .

(a) Calculate the **terminal pd** of the battery when the car is being started.

(b) If the headlamps are rated at  $12\text{ V}$ ,  $36\text{ W}$ , what is their **resistance** ?

(c) Calculate the value of their **power output** when the starter motor is in operation.


1 (a) On which conservation laws are **Kirchhoff's first and second laws** based ?

(b) For the circuit shown opposite, calculate :

(i) The **pd across the  $125\ \Omega$  resistor**.


(ii) The **pd across resistor R**.

(iii) The **resistance of resistor R**.

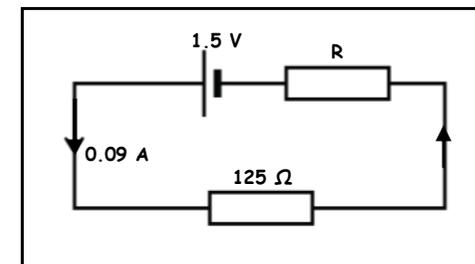

2 (a) State **Kirchhoff's Second Law**.

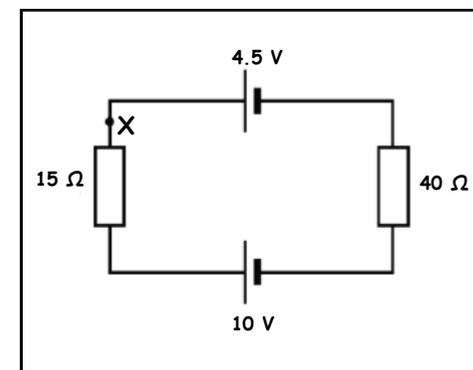(b) Apply Kirchhoff's Second Law to the circuit shown opposite to determine the **current at point X**.



3 You are given three resistors of resistance  $4\ \Omega$ ,  $6\ \Omega$  and  $8\ \Omega$ . Using all the resistors **draw** the combination to give :


(a) The **largest** resistance.

(b) The **smallest** resistance.

In each case calculate the **total resistance** of the combination.

4 (a) State Kirchoff's First Law.

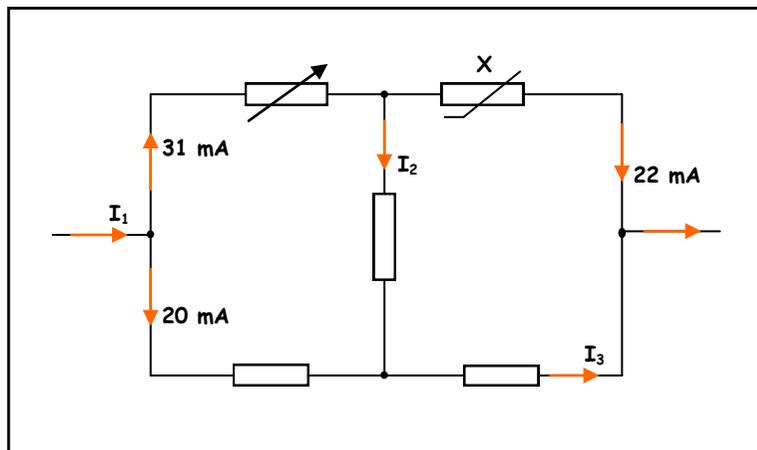(b) The diagram below shows part of an electrical circuit.



(i) Name the component marked X.

(ii) Determine the magnitude of the currents  $I_1$ ,  $I_2$  and  $I_3$ .


*(OCR AS Physics - Module 2822 - January 2004)*

5 The results of an experiment to determine the **emf (E)** and **internal resistance (r)** of a power supply are given in the table below.

V/V	1.43	1.33	1.18	1.10	0.98
I/A	0.10	0.30	0.60	0.75	1.00

Plot a suitable graph and use it to find E and r.

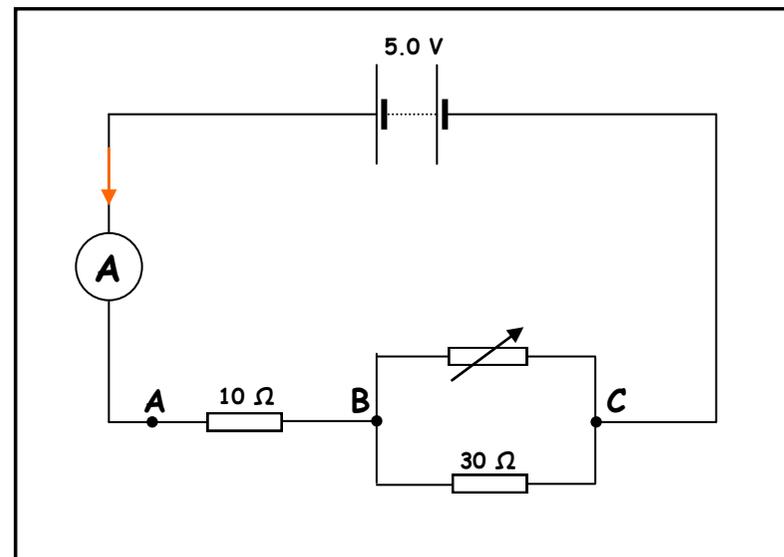6 The diagram below shows a circuit diagram including three resistors.



(a) The variable resistor is set on its maximum resistance of  $20 \Omega$ .

Calculate the resistance between points :

(i) B and C.

(ii) A and C.

(b) In the circuit shown in the diagram above, the battery has negligible internal resistance and an emf of  $5.0 \text{ V}$ . The variable resistor is now set on its lowest resistance of  $0 \Omega$ .

Calculate the **reading on the ammeter**.

*(OCR AS Physics - Module 2822 - January 2006)*